


NandSim

Digital Logic Circuit Simulator

Svendeprøve
Simon From Jakobsen
Juni 2026


Integrerede kredsløb

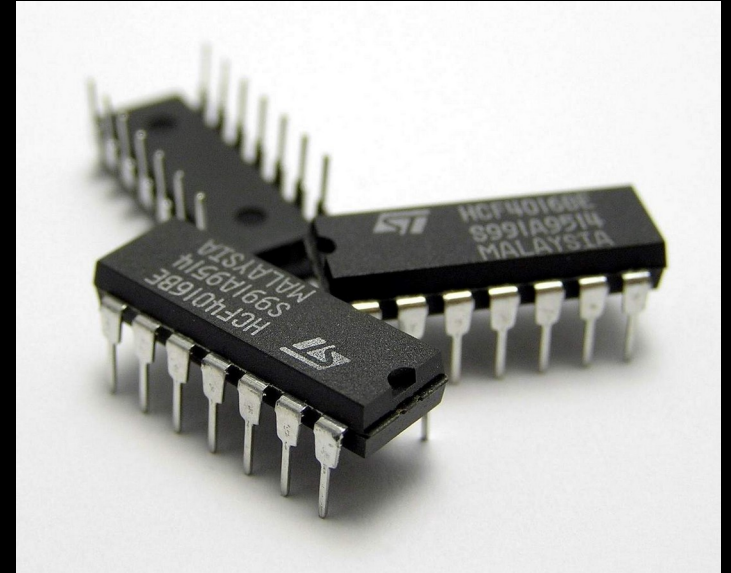- Elektroniske kredsløb
 - ledninger, komponenter, strøm, spænding
- Fotolitografi
- Formål, fx digital-logik
- Samlet pakke
 - inkluderer ofte software



Digital-logik


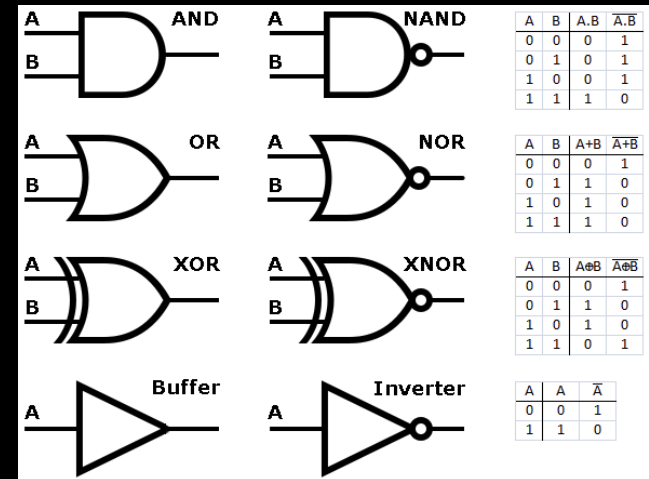
- Digital elektronik
- Binære værdier (1 eller 0, sandt eller falsk...)
- Logik-gates: *AND*, *OR*, *NOT*, ...
- Boolesk algebra: \wedge , \vee , \neg , ...
- Komponering
- Computing



Integreret software

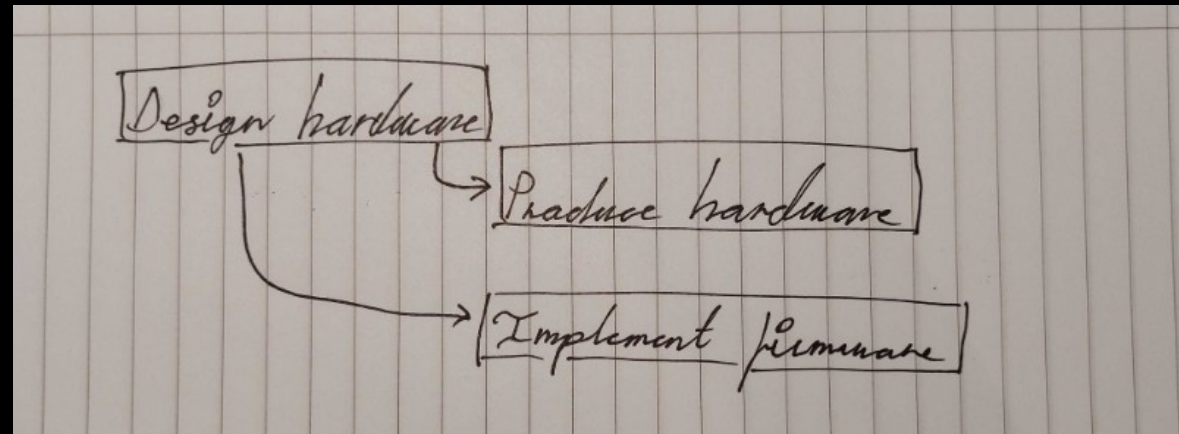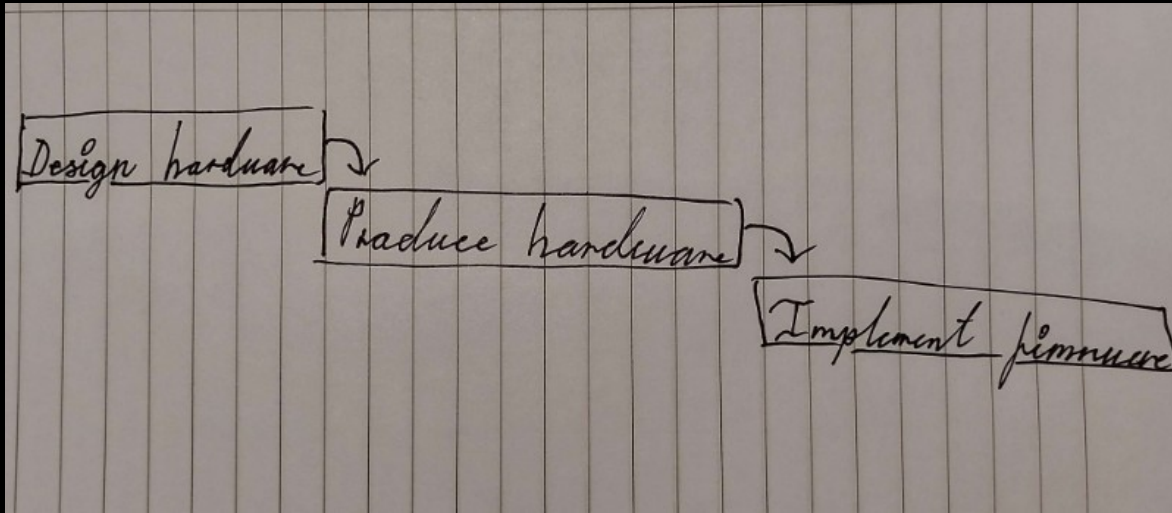- Firmware
- Drivers
- HAL
- RTOS
- Microcode
- Dataset





nandsim

nandsim — Mozilla Firefox Private Browsing

Private browsing

nandsim.sjfa.dk

150%

Save

Rename

Close

Toolbar

input

output

and

or

not

(Unnamed)

+

input (off)

input (off)

and


output (off)

```
graph LR; I1[input (off)] --> A[and]; I2[input (off)] --> A; A --> O[output (off)];
```


<https://nandsim.sfja.dk/>

Video af demonstration


XOR

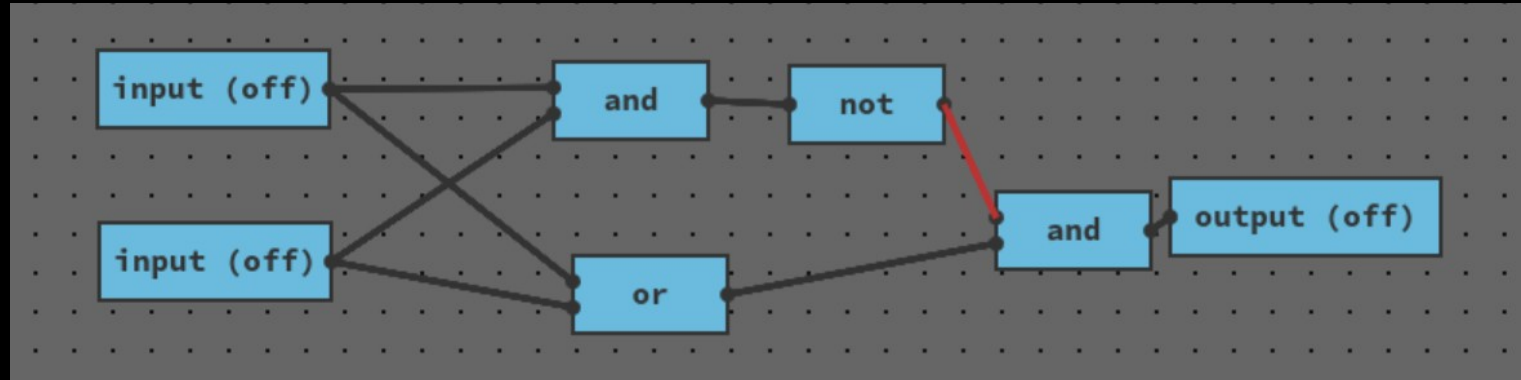


HALF ADDER

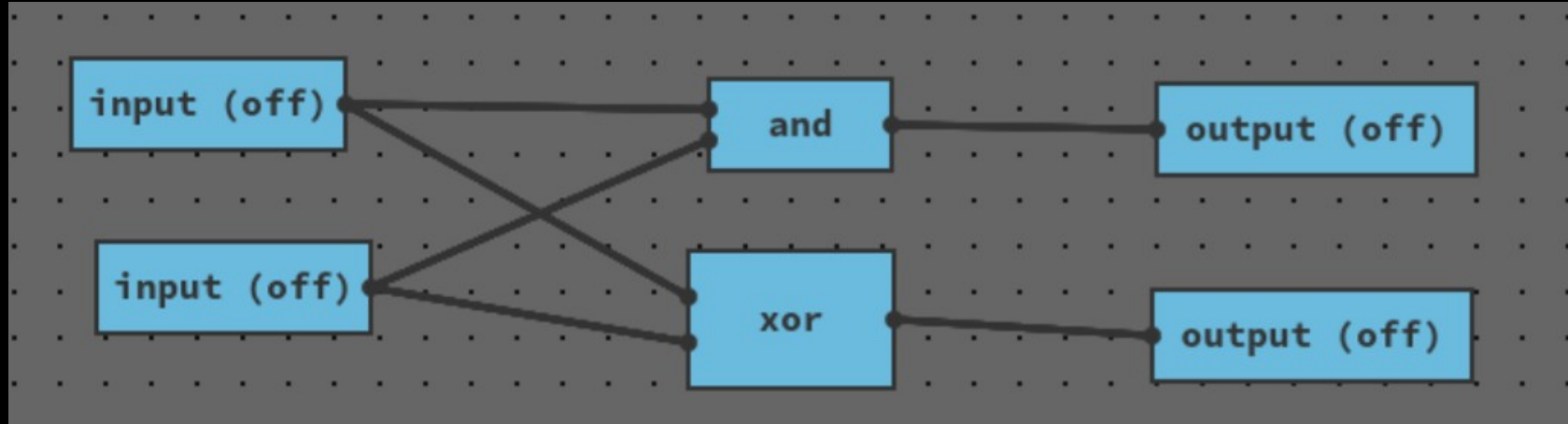


FULL ADDER

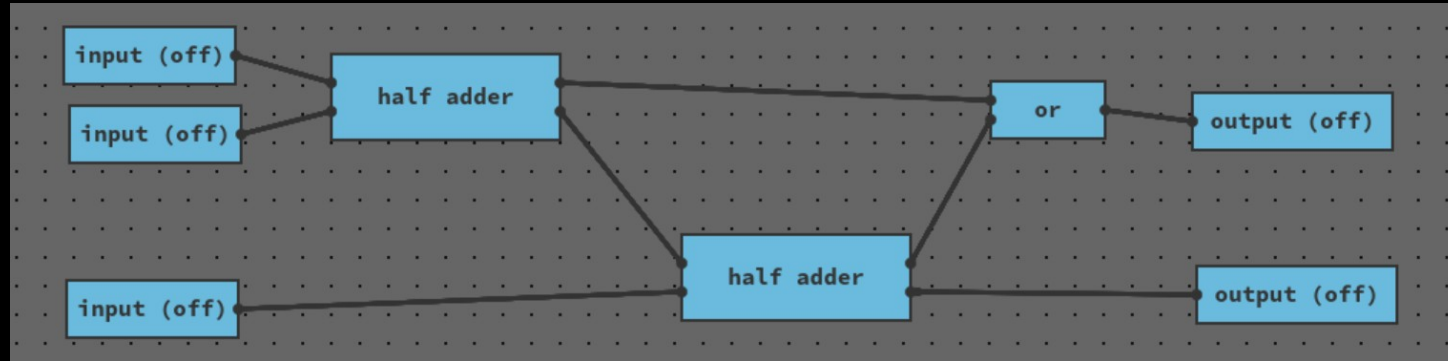

4-bit ADDER

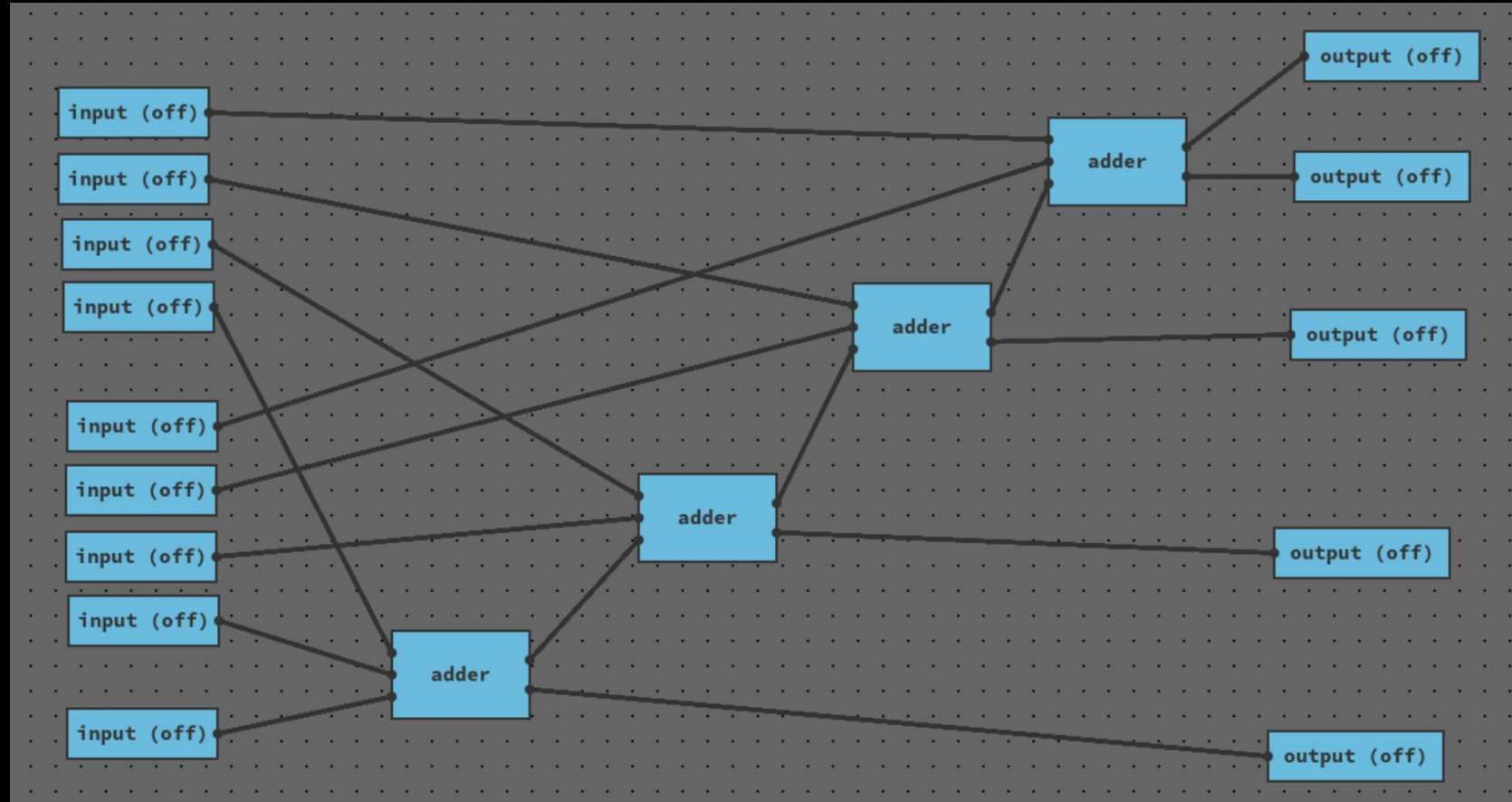

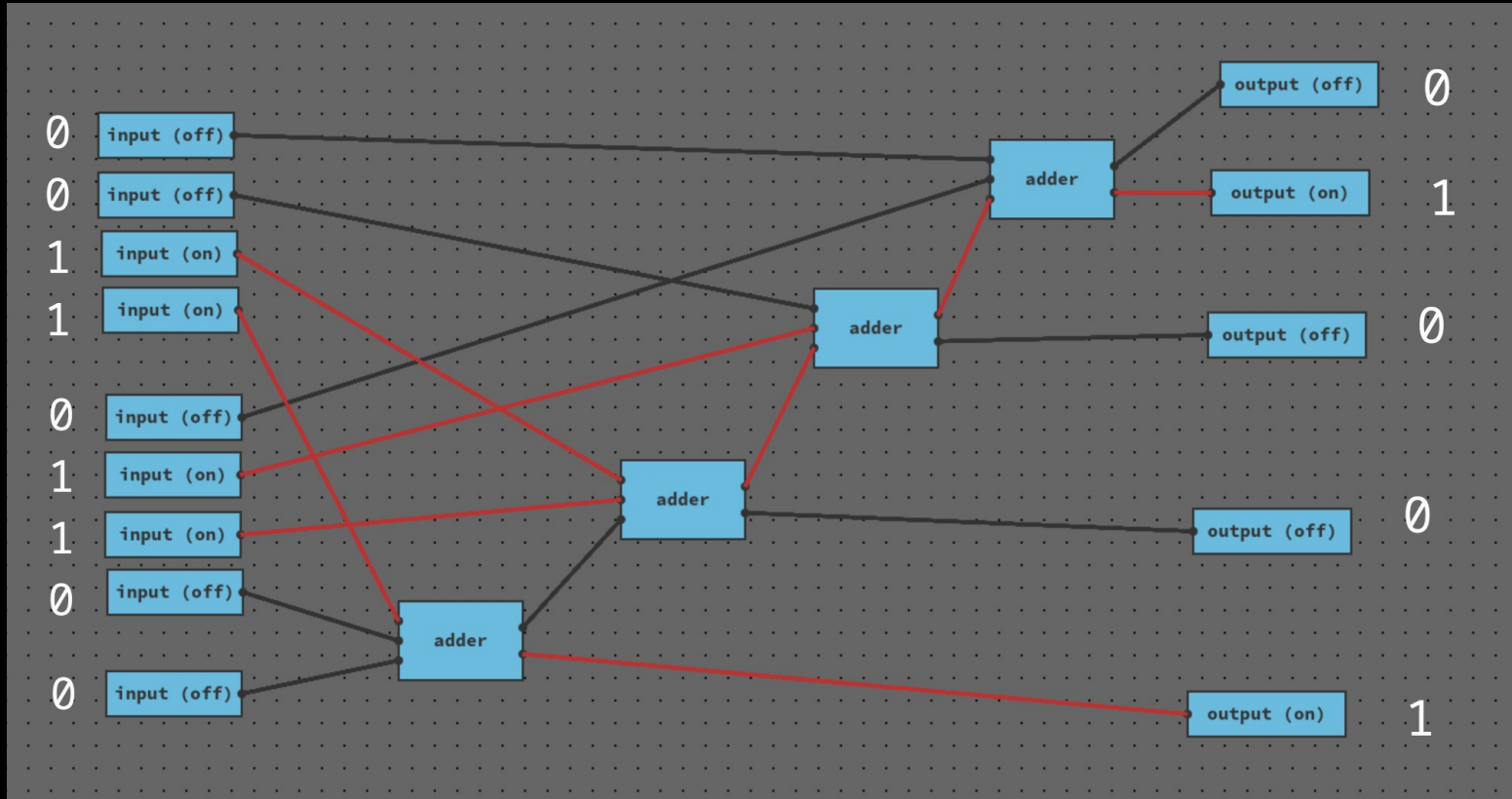


$$3 = 0011$$

$$6 = 0110$$

$$\begin{array}{r} 0011 \\ + 0110 \\ \hline = 1001 \end{array}$$

$$1001 = 9$$

$$3 + 6 = 9$$

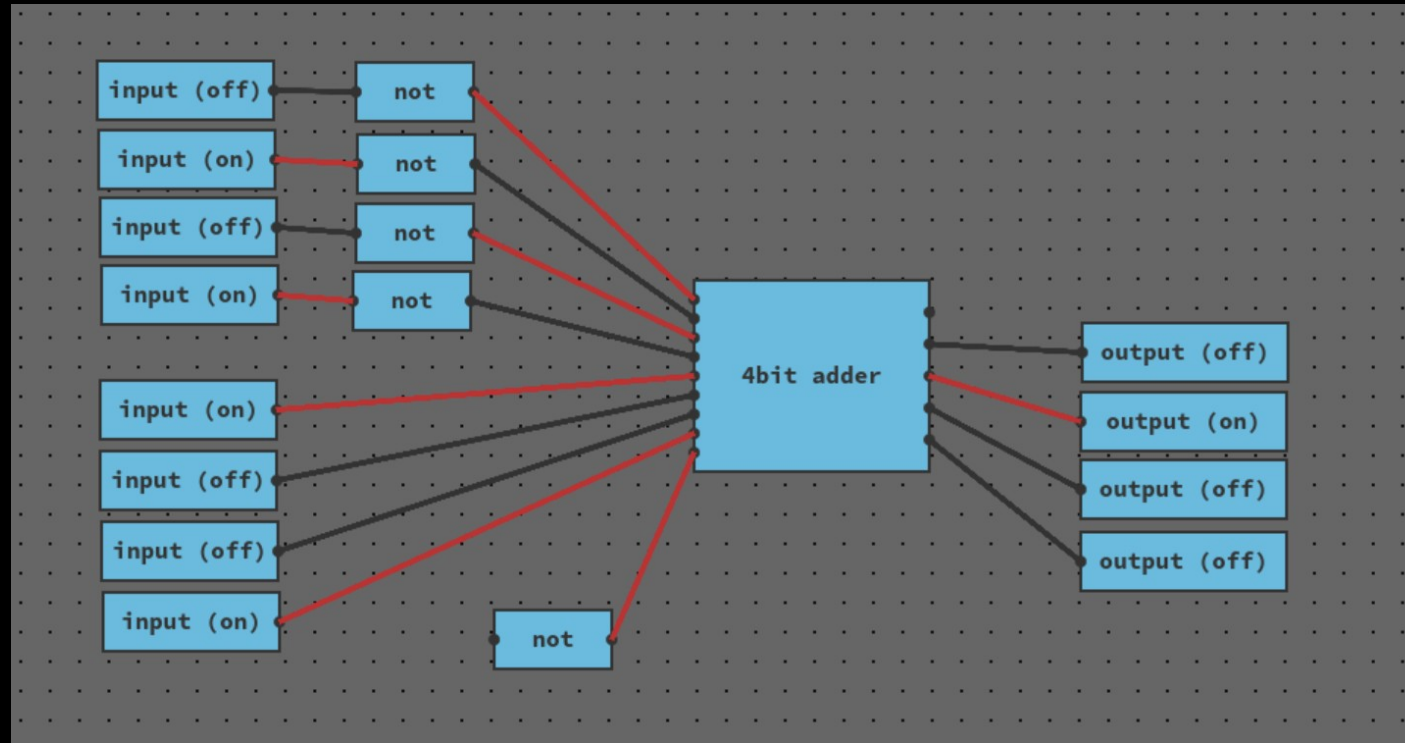


5 = 0101
9 = 1001


9 - 5 = 4

4 = 0100


Editor'en

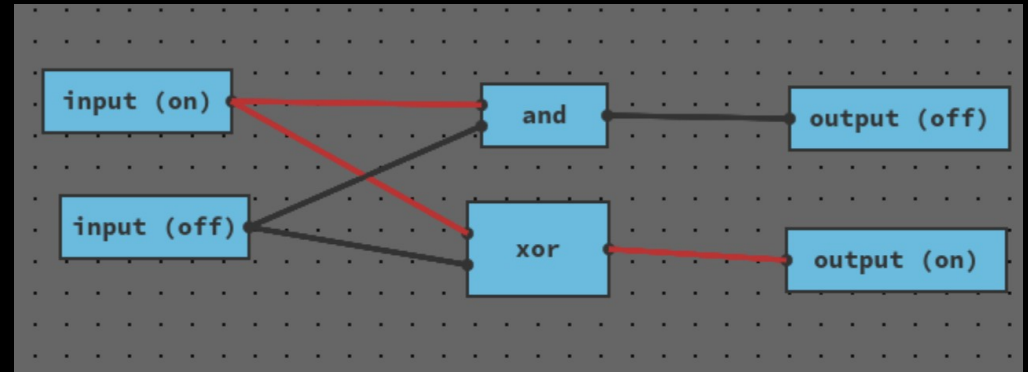- Visuel
- Kamera
- Selection
- Interaktion
- Flere modes




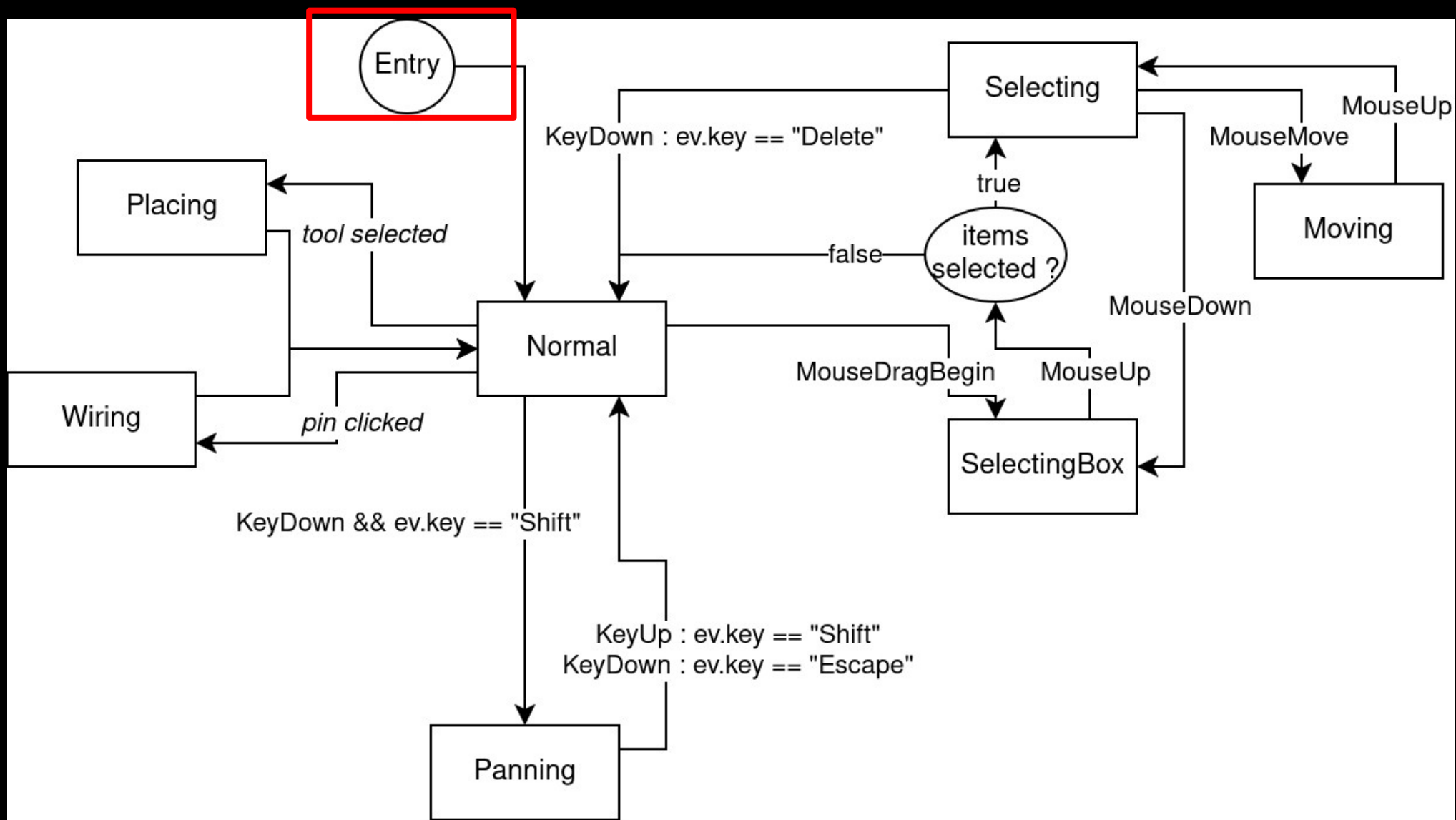


Mouse

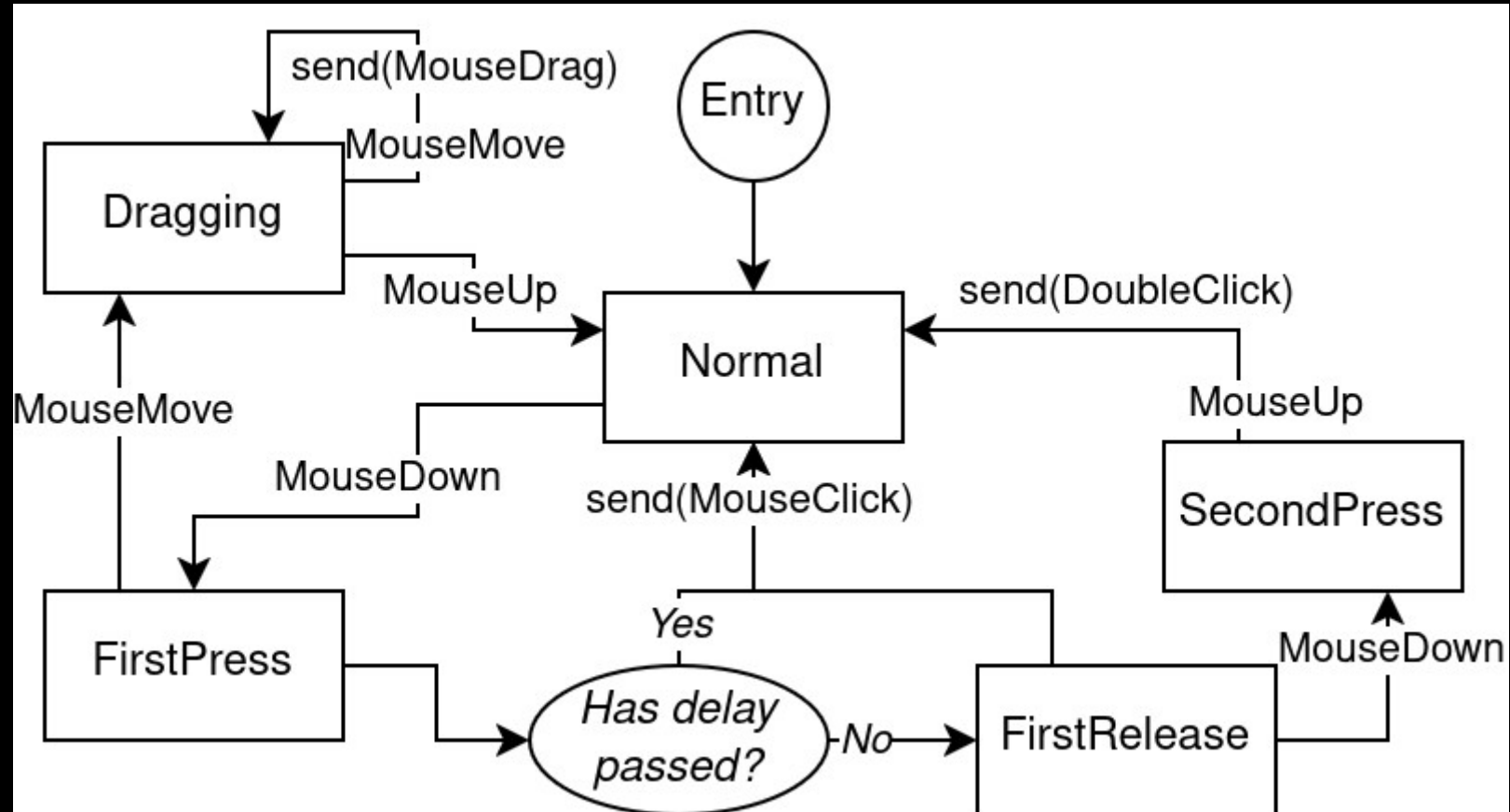


IR / Simulation

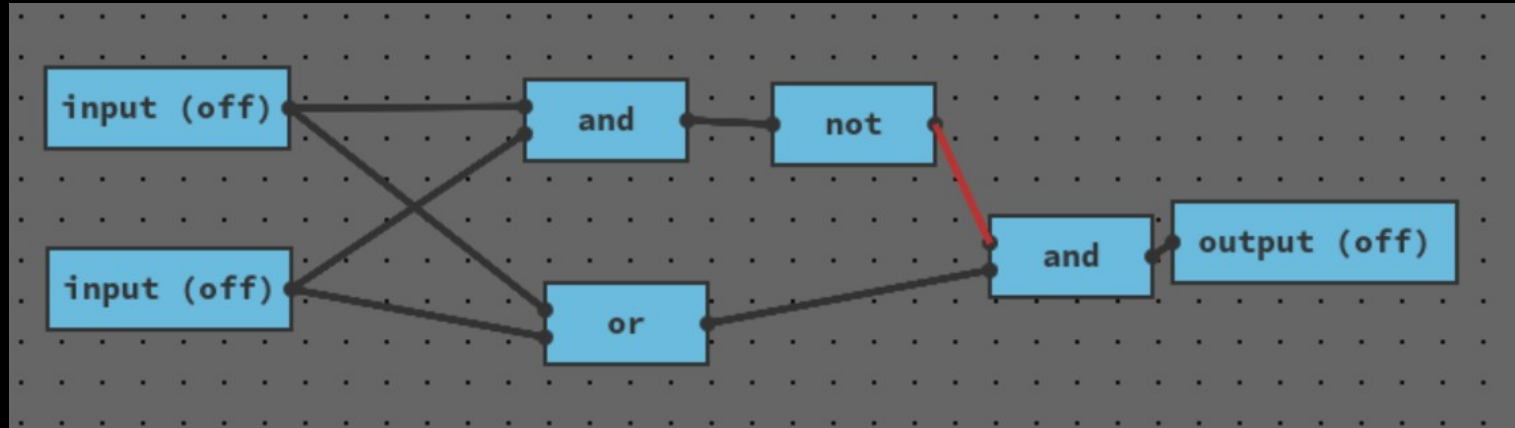
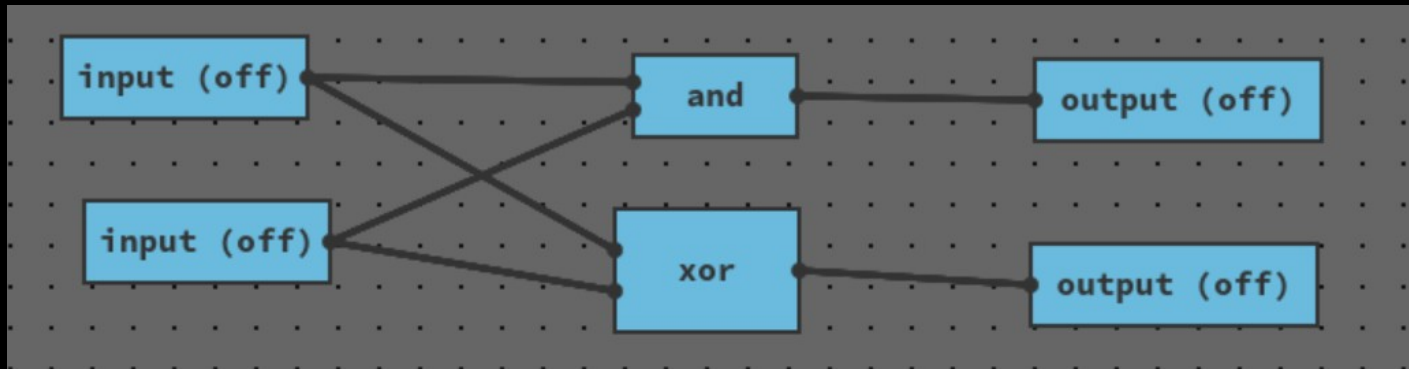
```
component xor 2 1 {  
  state [ ]  
  %0 = Input 0  
  %1 = Input 1  
  %2 = Nand %0, %1  
  %3 = Or %0, %1  
  %4 = And %2, %3  
  Output 0, %4  
}
```



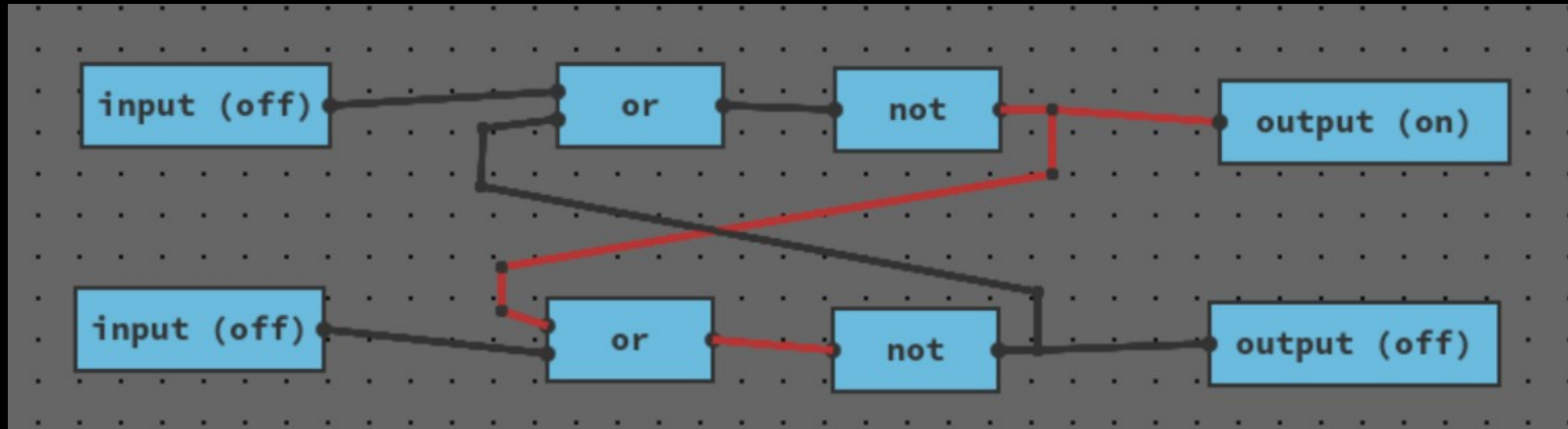
```
component half adder 2 2 {  
    state [ ]  
    %0 = Input 0  
    %1 = Input 1  
    %2 = Call xor (%0, %1)  
    %3 = Elem %2, 0  
    Output 1, %3  
    %4 = And %0, %1  
    Output 0, %4  
}
```



```
component rs latch 2 2 {  
    state [ #0 ]  
    %0 = Input 0  
    %1 = Input 1  
    %2 = GetState #0  
    %3 = Nor %0, %2  
    %4 = Nor %3, %1  
    SetState #0, %4  
    Output 1, %4  
    Output 0, %3  
}
```

```
412  
413 eliminateUnusedStmts() {  
414     const mut = new StmtMutater(this.comp, this.replacedStates);  
415  
416     const useCount = new Map<Stmt, number>();  
417     for (const stmt of mut) {  
418         for (const src of stmt.sources()) {  
419             useCount.set(src, (useCount.get(src) ?? 0) + 1);  
420         }  
421     }  
422  
423     const nonEffectfulStmts = new Set<StmtKind["tag"]>([  
424         "And", "Or", "Nand", "Nor", "Elem", "Input", "GetState", "Null",  
425     ]);  
426  
427     for (const stmt of mut) {  
428         if (!useCount.get(stmt) && nonEffectfulStmts.has(stmt.kind.tag)) {  
429             mut.removeStmt(stmt);  
430         }  
431     }  
432 }  
433
```

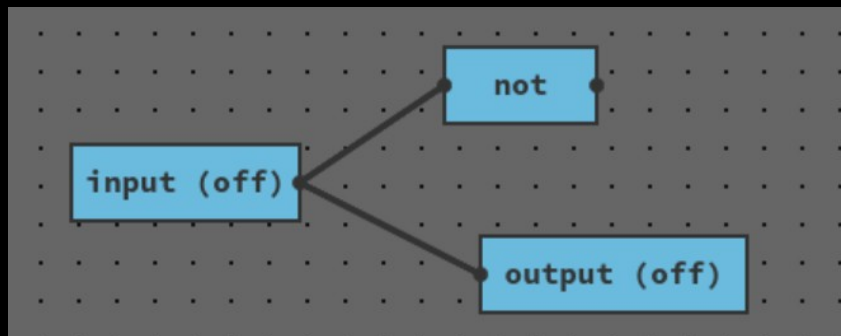

```
component <main> 1 1 {  
  state [ #0 ]  
  %0 = Input 0  
  %1 = Not %0  
  Output 0, %0  
}
```

An orange arrow points to the line `%1 = Not %0` in the code block.

```
component <main> 1 1 {  
  state [ #0 ]  
  %0 = Input 0  
  Output 0, %0  
}
```

```

26   for (let i = 0; i < comp.stmts.length; ++i) {
27       const stmt = comp.stmts[i];
28       const k = stmt.kind;
29       switch (k.tag) {
30           case "Null":
31               regs[i] = false;
32               break;
33           case "Input":
34               regs[i] = inputs[k.i];
35               break;
36           case "Output":
37               outputs[k.i] = regs[stmtIds.get(k.src)!];
38               break;
39 >       case "GetState": ...
49 >       case "SetState": { ...
59           }
60       case "Not":
61           regs[i] = operation((v) => !v, k.op);
62           break;
63       case "And":
64           regs[i] = operation((a, b) => a && b, k.lhs, k.rhs);
65           break;
66       case "Or":
67           regs[i] = operation((a, b) => a || b, k.lhs, k.rhs);
68           break;
69       case "Nand":
70           regs[i] = operation((a, b) => !(a && b), k.lhs, k.rhs);
71           break;
72       case "Nor":
73           regs[i] = operation((a, b) => !(a || b), k.lhs, k.rhs);
74           break;
75 >       case "Call": { ...
85           }
86 >       case "Elem": { ...
93           }


```


Ting der kan forbedres

- Musefunktioner virker suboptimalt
- Man kan ikke zoome
- Tabs og save-funktionalitet har huller
- Wire-stilen er grim
- Event-systemet er rodet


Ting jeg ikke nåede

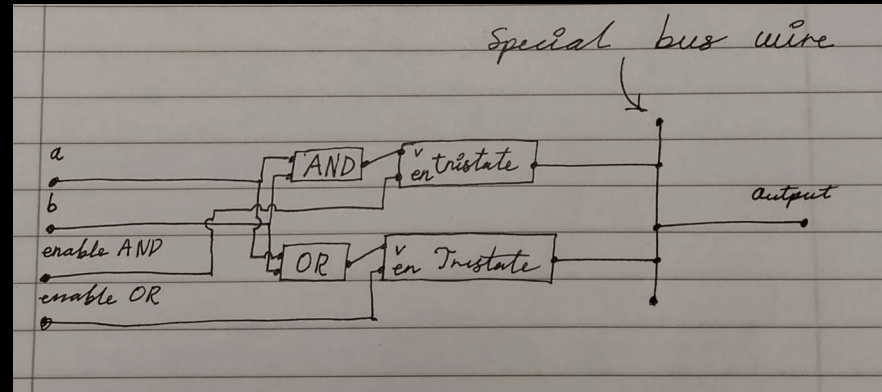- Importering af data
- Cloud-miljø
- CI-setup
- Native-afvikling
- Low impedance/Tri-state





Konklusion


half adder:

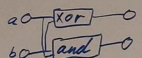


full adder:

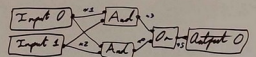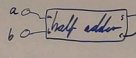

In this case collapse the And's.

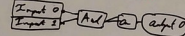


XOR:

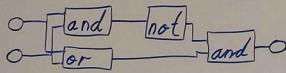

input a, b, c, d
e = and a, b
f = and c, d

$\{e, f\} = \text{and}\{a, b\}, \{c, d\}$

ac
0000
b d
0000
e f
0000

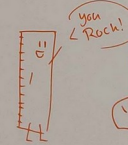

#KARNAUGH

component a

input x1, x2, x3, x4
x5, x6 = xor x1, x2, x3, x4
x7 = xor x5, x6
output x7

component xor2

input x1, x2, x3, x4
x5 = xor x1, x3
x6 = xor x2, x4
output x5, x6

TOPSDAG:

- STOLE OP
- LEDNINGER VÆK FRA GULVE K.A.T.


Mags-000

Merc1234!

SPS koordination, Katrine

Kaso (Skriver gerne på Teams)

MIS.

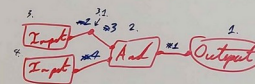

Forward traverse

1. x1 = Input 0
2. x2 = Input 1
3. x3 = Input 2
200. x200 = Input 199

Can I handle the SubStates?